

Design and Verification of Universal Asynchronous Receiver Transmitter (UART) Protocol

(by Ch.Anirudh)

1.Introduction:

Universal Asynchronous Receiver-Transmitter (**UART**) is a widely used communication protocol that enables serial data transfer between devices. Unlike synchronous communication protocols, UART does not require a shared clock between the transmitter and receiver, making it simple and efficient for data exchange over short distances. It is commonly used in **embedded systems, microcontrollers**, and computer peripherals for serial communication.

UART operates by transmitting data one bit at a time over a single data line. It consists of two main components: **UART Transmitter (TX)** and **UART Receiver (RX)**. The transmitter converts parallel data into a serial stream, while the receiver reconstructs the original parallel data. A **baud rate generator** controls the transmission speed, ensuring **proper synchronization** between the sender and receiver.

This project implements a complete **UART protocol**, including the transmitter, receiver, baud rate generator, and a protocol module. The design is verified through simulation and synthesis, ensuring correct data transmission and reception. The implementation adheres to standard UART specifications and can be used in various real-world applications such as embedded systems, IoT devices, and industrial automation.

2.Overview:

This project focuses on designing and implementing a **UART protocol** using Verilog/SystemVerilog. The system consists of the following major components:


- **UART Transmitter (TX):** Converts parallel data into a serial stream.
- **UART Receiver (RX):** Converts the received serial data back into parallel format.
- **UART Protocol Module:** Manages the communication process between TX and RX.
- **Baud Rate Generator:** Ensures data transmission at a predefined speed.
- **Testbenches:** Verifies the functionality of individual modules and the complete UART system.

The design is simulated and synthesized to verify its correctness and efficiency.

 3.Design and Implementation:

The UART protocol is designed using **Verilog/SystemVerilog** with a modular approach, ensuring flexibility and ease of debugging. The system consists of a **UART Transmitter (TX)**, which converts parallel data into a serial stream by adding start and stop bits, and a **UART Receiver (RX)**, which detects the start bit, samples the incoming data, and reconstructs it into parallel format. A **Baud Rate Generator** ensures synchronized communication by generating clock signals at the desired transmission speed. The **UART Protocol Module** manages data flow and ensures proper handshaking between the transmitter and receiver. The design is verified using **SystemVerilog testbenches**.

- **Transmitter (TX):**
 - Accepts an 8-bit parallel data input.
 - Adds start and stop bits.
 - Sends data bit-by-bit through tx_serial.
- **Receiver (RX):**
 - Detects the start bit.
 - Samples the incoming bits based on the baud rate.
 - Reconstructs the parallel data output.
- **Baud Rate Generator:**
 - Generates the clock signal for data sampling.
 - Configurable to support different baud rates.




Fig(a): UART Communication Wiring

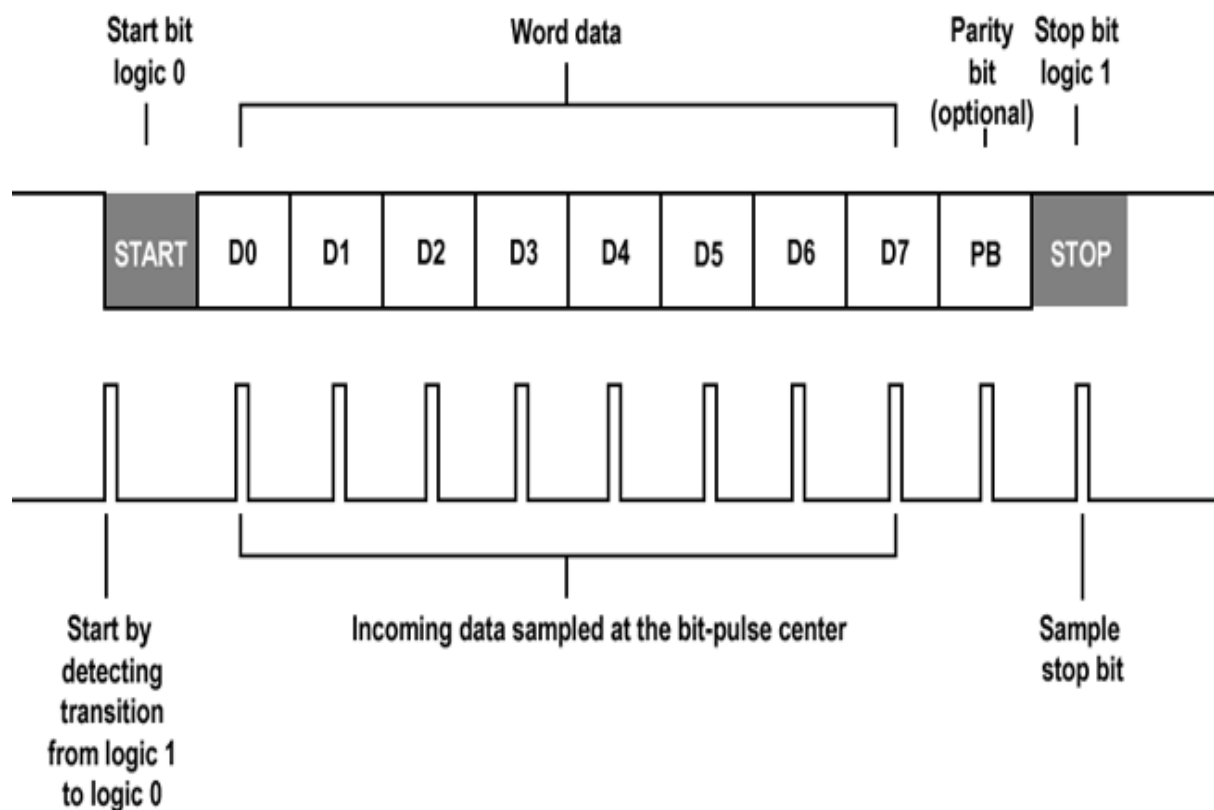4. Operations

- **Data Transmission:** The TX module converts the parallel input into a serial bit stream with start and stop bits.
- **Data Reception:** The RX module samples the serial data and reconstructs it into parallel format.
- **Baud Rate Synchronization:** The baud rate generator ensures both TX and RX operate at the same frequency.
- **Handshake Mechanism:** Ensures proper communication between sender and receiver.

The system is tested with different data values to confirm accurate transmission and reception.



Fig(b): UART Frame

5.RTL Code UART TX:

```
module uart_tx1 (
    input wire clk,
    input wire rst,
    input wire baud_tick,
    input wire [7:0] data_in,
    input wire send,
    output reg tx_serial,
    output reg tx_done
);

typedef enum logic [2:0] {IDLE, START, DATA, STOP} state_t;
state_t current_state, next_state;

reg [3:0] bit_index; // To track the current bit being sent
reg [7:0] shift_reg; // Shift register for data transmission

// State transition logic
always_ff @(posedge clk or posedge rst) begin
    if (rst) begin
        current_state <= IDLE; // Initialize to IDLE on reset
        tx_serial <= 1; // Idle state is high
        tx_done <= 0; // Reset tx_done
        bit_index <= 0; // Reset bit index
    end else begin
        current_state <= next_state; // Update current state on clock edge
    end
end

// State machine logic
always_comb begin
    // Default assignments to avoid latches
```

```

next_state = current_state;

case (current_state)
  IDLE: begin
    if (send) begin
      next_state = START; // Transition to START on send
    end
  end

  START: begin
    next_state = DATA; // Transition to DATA after start bit
  end

  DATA: begin
    if (baud_tick) begin
      if (bit_index == 7) begin
        next_state = STOP; // Move to STOP after the last data bit
      end
    end
  end

  STOP: begin
    if (baud_tick) begin
      next_state = IDLE; // Return to IDLE after stop bit
    end
  end

  default: next_state = IDLE;
endcase

end

// Output and data handling
always_ff @(posedge clk) begin

```

```

case (current_state)
  IDLE: begin
    tx_done <= 0;
    if (send) begin
      shift_reg <= data_in; // Load data
      bit_index <= 0;
      tx_serial <= 1; // Idle state for serial line
    end
  end

  START: begin
    tx_serial <= 0; // Start bit
  end

  DATA: begin
    if (baud_tick) begin
      tx_serial <= shift_reg[bit_index]; // Transmit current bit
      bit_index <= bit_index + 1; // Move to next bit
    end
  end

  STOP: begin
    if (baud_tick) begin
      tx_serial <= 1; // Stop bit
      tx_done <= 1; // Indicate completion
    end
  end
endcase
end

endmodule

```

UART RX:

```
module uart_rx1 (  
    input wire clk,  
    input wire rst,  
    input wire rx_serial,  
    input wire baud_tick,  
    output reg [7:0] data_out,  
    output reg rx_done  
);  
  
typedef enum logic [2:0] {IDLE, START, DATA, STOP} state_t;  
state_t current_state, next_state;  
  
reg [3:0] bit_index; // To track the current bit being received  
reg [7:0] shift_reg; // Shift register for received data  
  
// State transition logic  
always_ff @(posedge clk or posedge rst) begin  
    if (rst) begin  
        current_state <= IDLE; // Initialize to IDLE on reset  
        rx_done <= 0; // Reset rx_done  
        shift_reg <= 0; // Reset shift register  
        bit_index <= 0; // Reset bit index  
        $display("Time: %0t | Reset: Moving to IDLE state", $time);  
    end else begin  
        current_state <= next_state; // Update current state on clock edge  
    end  
end  
  
// State machine logic  
always_ff @(posedge clk) begin  
    case (current_state)  
        IDLE: begin
```



```

rx_done <= 0; // Reset rx_done in IDLE

if (~rx_serial) begin // Start bit is low
    next_state <= START;

    $display("Time: %0t | Start bit detected, moving to START state", $time);
end else begin
    next_state <= IDLE;
end
end

START: begin
    if (baud_tick) begin
        next_state <= DATA; // Move to data state after start bit
        bit_index <= 0; // Reset bit index
        $display("Time: %0t | Start bit received", $time);
    end else begin
        next_state <= START; // Wait for baud tick
    end
end

DATA: begin
    if (baud_tick) begin
        shift_reg <= {rx_serial, shift_reg[7:1]}; // Shift in the received bit
        $display("Time: %0t | Received Data Bit %b: %b", $time, bit_index, rx_serial);
        if (bit_index == 7) begin
            next_state <= STOP; // Move to STOP state
            $display("Time: %0t | Last data bit recieved, moving to stop state", $time);
        end else begin
            bit_index <= bit_index + 1;
            next_state <= DATA;
        end
    end else begin
        next_state <= DATA; // Wait for baud tick
    end
end

```

```

end

STOP: begin
    if (baud_tick) begin
        if (rx_serial == 1) begin // Stop bit high
            data_out <= shift_reg; // Load received data
            rx_done <= 1; // Indicate reception done
            $display("Time: %0t | Stop bit received, data_out: %h", $time, data_out);
        end else begin
            $display("Time: %0t | Error: Stop bit not high", $time);
        end
        next_state <= IDLE; // Move back to IDLE
    end else begin
        next_state <= STOP; // Wait for baud tick
    end
end

default: next_state <= IDLE;

endcase
end
endmodule

```

BAUD RATE Generator:

```

module baud_generator #(parameter BAUD_RATE = 9600, CLOCK_FREQ = 50000000)
(
    input wire clk,
    input wire rst,
    output reg baud_tick
);
    localparam TICKS = CLOCK_FREQ / BAUD_RATE;
    reg [15:0] tick_counter;

    always @(posedge clk or posedge rst) begin

```

```

if (rst) begin
    tick_counter <= 0;
    baud_tick <= 0;
end else begin
    if (tick_counter == TICKS - 1) begin
        tick_counter <= 0;
        baud_tick <= 1;
    end else begin
        tick_counter <= tick_counter + 1;
        baud_tick <= 0;
    end
end
end
end

```

```
endmodule
```

UART Protocol:

```

module uart_protocol1#(parameter BAUD_RATE = 9600, CLOCK_FREQ = 50000000)(
    input wire clk,
    input wire rst,
    input wire [7:0] tx_data, //data to transmit
    input wire tx_start,    // signal to start transmission
    input wire rx_serial,   // serial input for rx
    output wire tx_serial,   // serial output for tx
    output wire [7:0] rx_data, // recieved data for output
    output wire tx_done,    // tx done flag
    output wire rx_done     // rx done flag
);
    //internal signals
    wire baud_tick;

    //instantiate baud generator
    baud_generator #(
        .BAUD_RATE (BAUD_RATE),

```

```

        .CLOCK_FREQ(CLOCK_FREQ)
    )baud_gen_inst(
        .clk (clk),
        .rst(rst),
        .baud_tick(baud_tick)
    );
//instantiate uart tx
uart_tx1 uart_tx_inst(.clk(clk),
    .rst(rst),
    .baud_tick(baud_tick),
    .data_in(tx_data),
    .send(tx_start),
    .tx_serial(tx_serial),
    .tx_done(tx_done)
);
// instantiate uart rx
uart_rx1 uart_rx_inst (.clk(clk),
    .rst(rst),
    .rx_serial(rx_serial),
    .baud_tick(baud_tick),
    .data_out(rx_data),
    .rx_done(rx_done)
);
endmodule

```

6.Test Benches:

UART Rx TB:

```

module tb1_uart;

    // Parameters for baud rate and clock frequency
    parameter BAUD_RATE = 9600;
    parameter CLOCK_FREQ = 50000000;

```

```

// Signals
reg clk;
reg rst;
reg rx_serial;
reg baud_tick;
wire [7:0] data_out;
wire rx_done;

// Instantiate the receiver module
uart_rx1 uut (
    .clk(clk),
    .rst(rst),
    .rx_serial(rx_serial),
    .baud_tick(baud_tick),
    .data_out(data_out),
    .rx_done(rx_done)
);

// Instantiate the baud generator
baud_generator #(
    .BAUD_RATE(BAUD_RATE),
    .CLOCK_FREQ(CLOCK_FREQ)
) baud_gen (
    .clk(clk),
    .rst(rst),
    .baud_tick(baud_tick)
);

// Clock generation
always #10 clk = ~clk; // 50 MHz clock

// Serial transmission task
task send_serial_data(input [7:0] data);

```

```

integer i;

begin
    // Send start bit (0)
    rx_serial = 0;
    @(posedge baud_tick);

    // Send 8 data bits (LSB first)
    for (i = 0; i < 8; i = i + 1) begin
        rx_serial = data[i];
        @(posedge baud_tick);
    end

    // Send stop bit (1)
    rx_serial = 1;
    @(posedge baud_tick);
end

endtask

// Testbench procedure
initial begin
    // Initialize signals
    clk = 0;
    rst = 1;
    rx_serial = 1; // Idle state for serial line
    #50 rst = 0; // Release reset

    // Wait for some time
    #100;

    // Transmit first byte: 0xAA
    $display("Time: %0t | Sending byte: 0xAA", $time);
    send_serial_data(8'hAA);
    wait(rx_done);

```

```

    #100;

    $display("Time: %0t | recieved byte: 0x%h | rx_done: %b", $time, data_out, rx_done);

    //end simulation

    #100;

    $finish;

end

```

```
endmodule
```

UART Protocol TB:

```

module tb_uart_protocol1;

    // Parameters

    parameter BAUD_RATE = 9600;

    parameter CLOCK_FREQ = 50000000;

    // Signals

    reg clk;

    reg rst;

    reg [7:0] tx_data;

    reg tx_start;

    wire tx_serial;

    wire [7:0] rx_data;

    wire tx_done;

    wire rx_done;

    reg rx_serial;

    // Clock generation

    initial begin

        clk = 0;

        forever #10 clk = ~clk; // 50 MHz clock

    end

```

```
// Instantiate the UART protocol module
```

```
uart_protocol1 #(
    .BAUD_RATE(BAUD_RATE),
    .CLOCK_FREQ(CLOCK_FREQ)
) uut (
    .clk(clk),
    .rst(rst),
    .tx_data(tx_data),
    .tx_start(tx_start),
    .tx_serial(tx_serial),
    .rx_serial(rx_serial),
    .rx_data(rx_data),
    .tx_done(tx_done),
    .rx_done(rx_done)
);
```

```
// Task for applying reset
```

```
task apply_reset();
    begin
        rst = 1;
        #200; // Hold reset for 100 ns
        rst = 0;
    end
endtask
```

```
// Task to send and verify UART data
```

```
task send_data(input [7:0] data_to_send);
    begin
        tx_data = data_to_send;
        tx_start = 1;
        #20 tx_start = 0; // Clear start signal

        wait(tx_done); // Wait until transmission is done
    end
endtask
```



```

        $display("Time: %0t | Sent Data: 0x%02h", $time, data_to_send);

        wait(rx_done); // Wait until reception is done
        if (rx_data == data_to_send) begin
            $display("Time: %0t | Received Data: 0x%02h | Test Passed", $time, rx_data);
        end else begin
            $fatal("Time: %0t | Received Data: 0x%02h | Test Failed", $time, rx_data);
        end
    end
endtask

// Loopback: Drive RX serial input with TX serial output
always @(posedge clk) begin
    rx_serial <= tx_serial;
end

// Testbench logic
initial begin
    $display("Starting UART Protocol Testbench...");


    // Apply reset
    apply_reset();

    // Test case 1: Send 0xAA
    send_data(8'hAA);

    // Simulation complete
    $display("Simulation Complete: All tests passed.");
    #500 $finish;
end
endmodule


```

7.Elaborated Design:

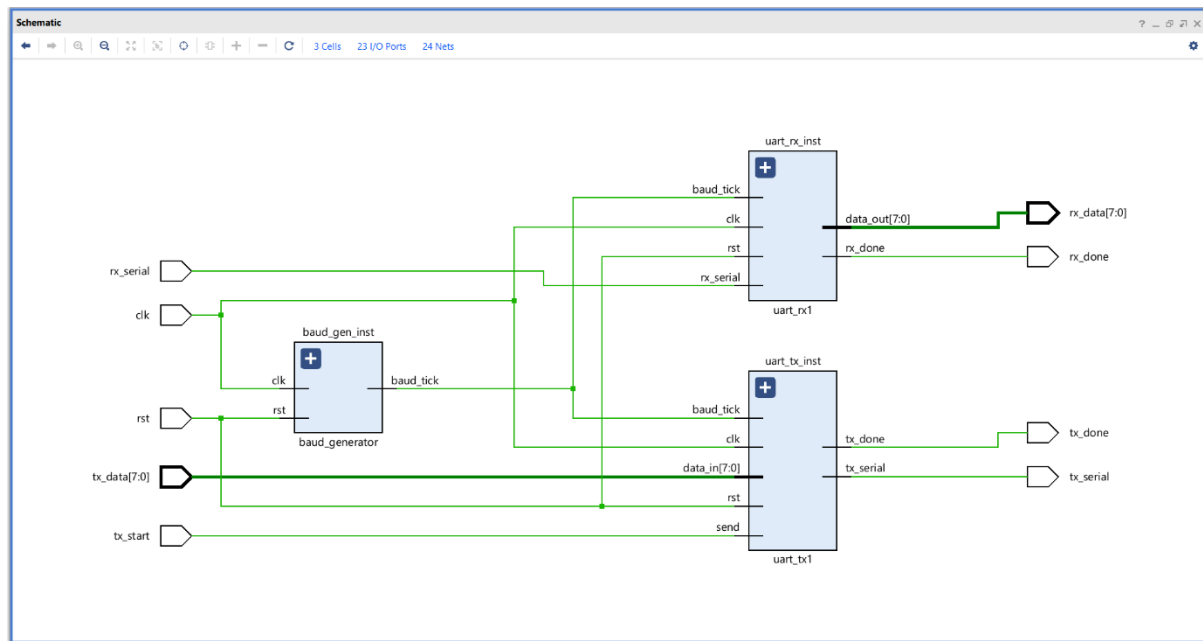


Fig(c): Elaborated design of UART

8.Simulations:

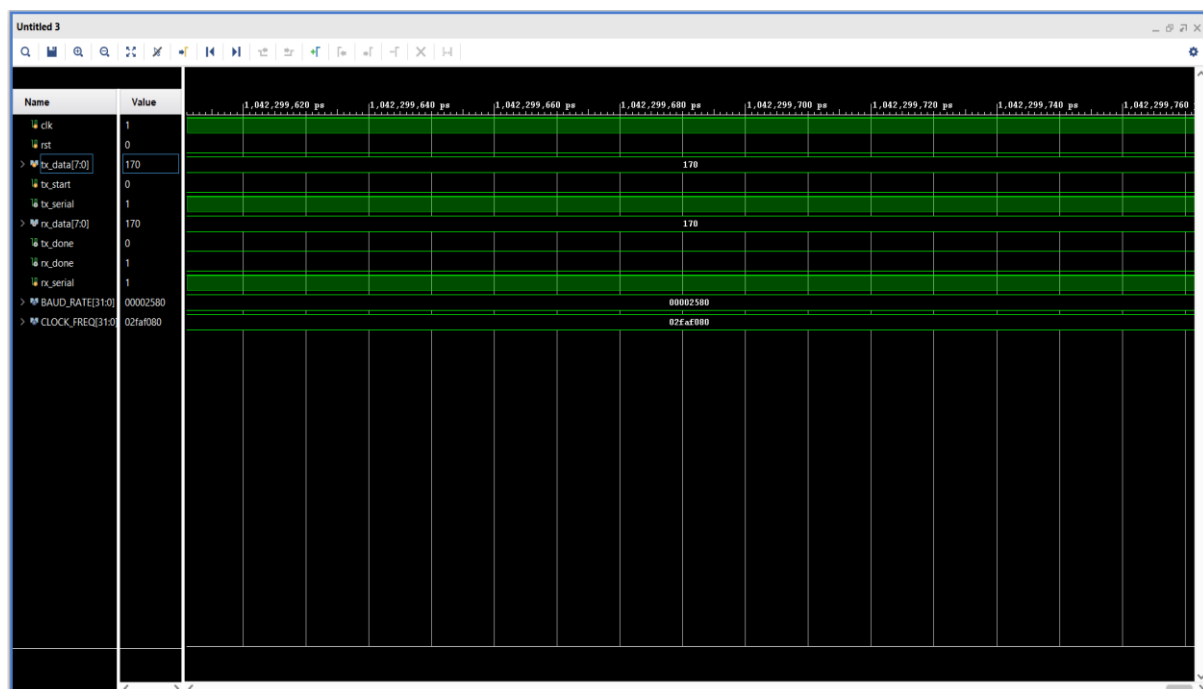


Fig(d): UART Simulation 1

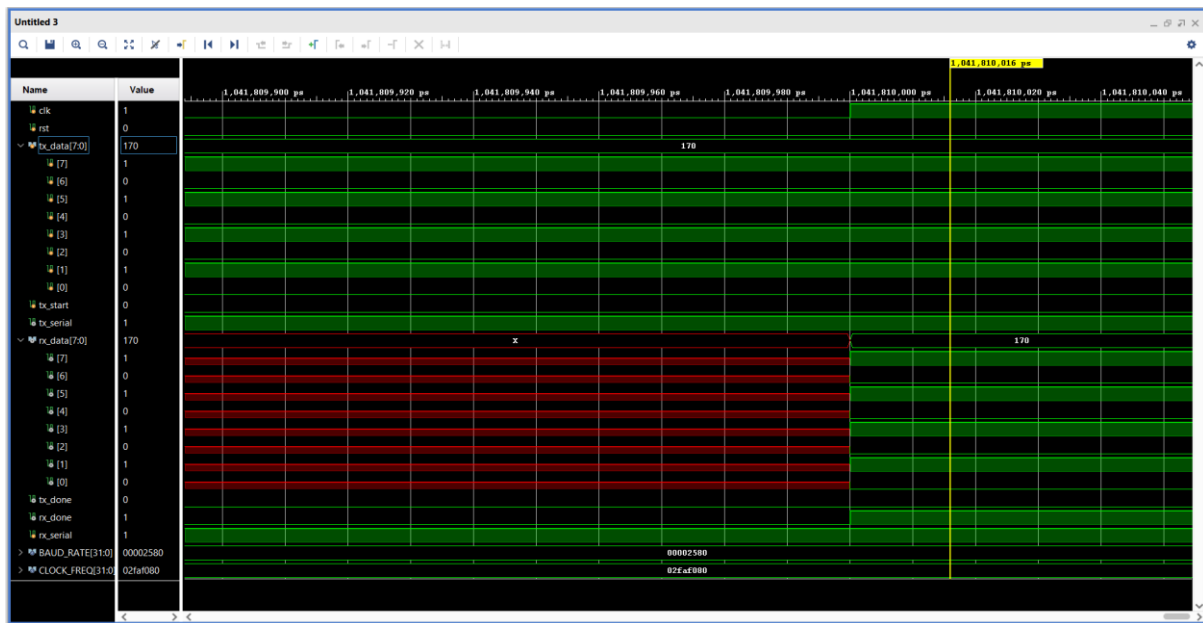

Fig(e): UART Simulation 2

9.Schematic

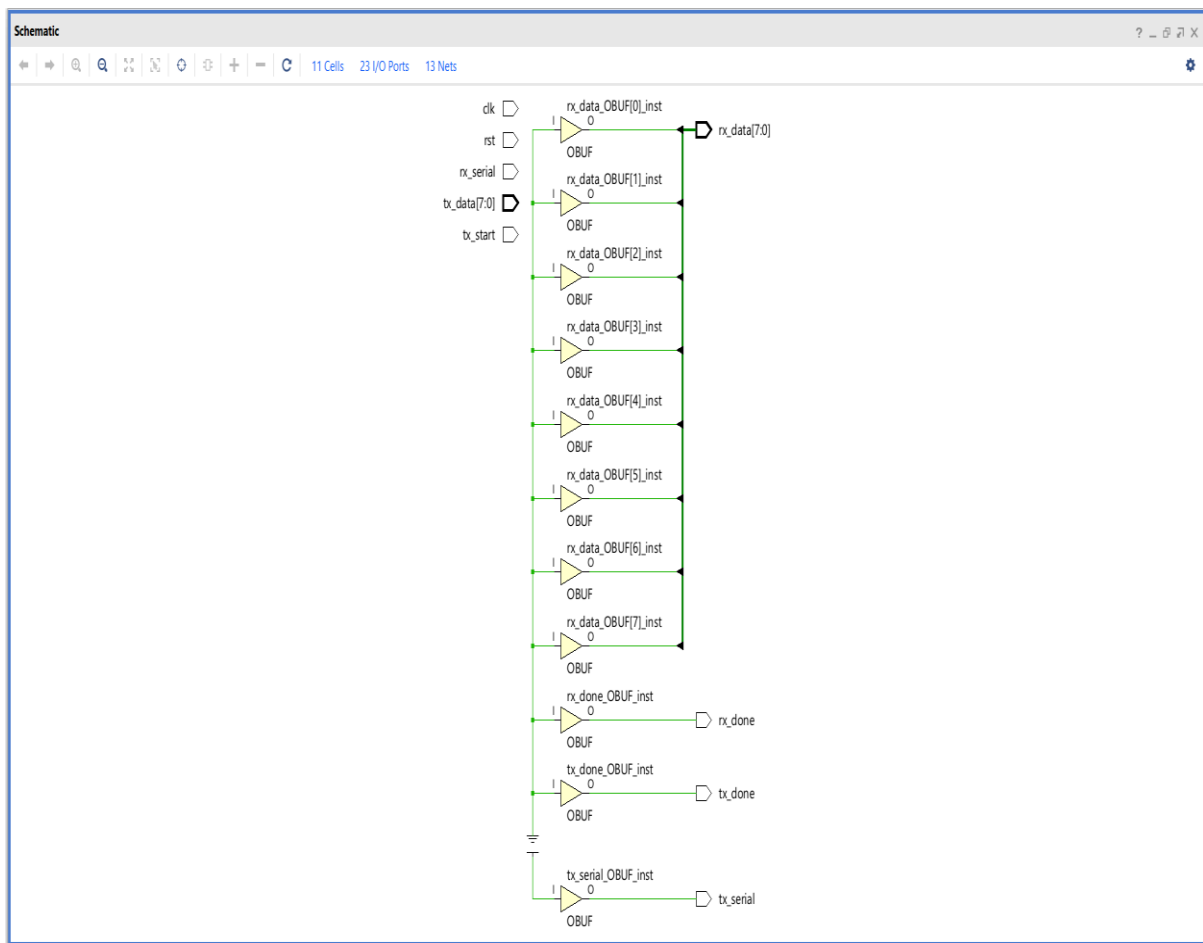

Fig(f): UART Schematic

10.Advantages:

- Simple and widely used protocol.
- No need for a shared clock between TX and RX.
- Low hardware complexity compared to SPI and I2C.
- Supports multiple baud rates.

Disadvantages:

- Slower compared to SPI and I2C.
- Limited to point-to-point communication.
- No built-in error detection (except optional parity bit).

11.Applications:

- Microcontrollers and Embedded Systems
- Serial Communication between Computers and Peripherals
- Industrial Automation and Control Systems
- Wireless Communication Modules (Bluetooth, GSM, GPS)
- Debugging and Firmware Uploading

12.Conclusion:

This project successfully implements a fully functional UART protocol, including TX, RX, baud rate generator, and testbenches. The design is validated through simulation and synthesis, confirming accurate data transmission and reception. UART remains a fundamental communication standard due to its simplicity and efficiency. This implementation can be further enhanced by adding error detection mechanisms and flow control for more robust communication.

---- The End--

